

Logic Gates and Their Differences

1. Functional Differences

| Gate | Symbol Description | Logical Expression | Output Behavior |
|------|---------------------------------|------------------------|---|
| AND | D-shaped gate | $Q = A \cdot B$ | High (1) only when both inputs are 1 |
| NAND | AND with output bubble | $Q = \neg(A \cdot B)$ | Low (0) only when both inputs are 1, otherwise high |
| OR | Curved input gate | $Q = A + B$ | High (1) when at least one input is 1 |
| NOR | OR with output bubble | $Q = \neg(A + B)$ | High (1) only when both inputs are 0 |
| XOR | OR with extra curved input line | $Q = A \oplus B$ | High (1) only when inputs are different |
| XNOR | XOR with output bubble | $Q = \neg(A \oplus B)$ | High (1) when inputs are the same |
| NOT | Triangle with output bubble | $Q = \neg A$ | Inverts the input |

2. Truth Table Overview

| A | B | AND | NAND | OR | NOR | XOR | XNOR |
|---|---|-----|------|----|-----|-----|------|
| 0 | 0 | 0 | 1 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 1 | 0 | 0 | 1 |

3. Circuit-Level Differences

- AND / NAND: Often implemented using series transistors (current flows only when both inputs are high).
- OR / NOR: Use parallel transistors (current flows if either input is high).
- XOR / XNOR: Combine AND, OR, and NOT gates internally; more complex transistor networks.
- NOT: Simplest gate, just one transistor stage.